

Name: .....

Email: .....

**Instructions**

# **.No Calculators!!**

- Make sure your exam is complete. There should be 9 pages including this cover sheet and a collection of figures.
- No Calculators, cell phones, or other electronic devices.
- All questions are equally weighted.
- Answer in the space provided if at all possible.
- If a question is unclear please ask early in the test.
- There is a Take Home question. It will be emailed today.
- Some Boolean Algebra Theorems are given in figures
- Good Luck!

1. (a) Convert Octal  $657.2_{10}$  to hexadecimal (to two “decimal” places)

(b) Convert  $173.745_8$  to hexadecimal.

(c) Convert  $A3.1AB_{16}$  to decimal using no calculator, leave your answer as an expression.

(d) Convert  $0000\ 1111\ 1111\ 0000\ 1111\ 1111\ 0000\ 0000_2$  to decimal. Express your answer as an expression that is a sum of terms of the form  $2^k$ .



3. Simplify boolean functions

(a) Simplify  $F(X,Y,Z)=\sum(0,2,3,7)$  in sums-of-products form.

(b) What is a non-essential implicant set? Give an example?

(c) Simplify  $F(A,B,C,D)=\Pi(3, 6, 7, 9, 11)$  in sums-of-products form, with don't care  $d(A,B,C,D)=\sum(10,12,13,14,15)$

4. (a) Simplify using Axioms  $F = A' \bullet B' \bullet C \bullet D + A' \bullet B' \bullet C \bullet D' + A' \bullet B \bullet C \bullet D + A' \bullet B \bullet C \bullet D' + A \bullet C \bullet D' + A \bullet B' \bullet C \bullet D'$

- (b) Why would a function have don't care conditions? Give an example.

5. (a) Draw a 4 to 1 multiplexer

(b) Show how to implement  $F(X,Y,Z)=\sum(0,4,6,7)$  using a decoder.

6. Carry Lookahead

(a) In a 14 pin package what are usually connected to pins 7 and 14?

(b) Give the formula for  $G_i$

(c) Give the formula for  $P_i$

(d) In a 5 bit carry look ahead unit what is the formula for  $G_{block}$  ?

(e) On figure F, show how to wire up  $G_i$  and  $P_i$

7. Identify from the collection of figures (extra handout)

(a) A.

(b) B.

(c) C

8. Show how to build a 11 to 1 multiplexer from 4 to 1 multiplexers.

9. (a) Explain how a transistor is turned on by placing a charge on the gate. Provide a drawing.

(b) Analyze the CMOS Circuit in figure D on the collection of figures but just for the one set of inputs asked for on the figure!!!!

(c) Draw a CMOS three input NOR



10. VHDL

(a) Give an VHDL entity section for a 1 to 4 demultiplexer

(b) Give a VHDL specification for Full Adder