

2 qubits.

$$\text{Qubit} = \left\{ a|0\rangle + b|1\rangle \mid a, b \in \mathbb{C}, |a|^2 + |b|^2 = 1 \right\}$$

Qubit  $\otimes$  Qubit

$$= \left\{ a|00\rangle + b|01\rangle + c|10\rangle + d|11\rangle \mid |a|^2 + |b|^2 + |c|^2 + |d|^2 = 1 \right\}$$

if  $|\varphi_1\rangle \in \text{Qubit}$

$|\varphi_2\rangle \in \text{Qubit}$

$$|\varphi_1\rangle \otimes |\varphi_2\rangle = |\varphi_1 \varphi_2\rangle = (a|0\rangle + b|1\rangle) \otimes (c|0\rangle + d|1\rangle)$$

the converse is not true.


Note that ~~if~~ if  $\psi \in \text{Qubit} \otimes \text{Qubit}$ .

$\psi$  need not be separable, i.e.

$$\psi = |\varphi_1\rangle \otimes |\varphi_2\rangle,$$


e.g.  $\frac{1}{\sqrt{2}}(|00\rangle + |11\rangle)$  can not be written as ~~is~~  $|\varphi_1\rangle \otimes |\varphi_2\rangle$ .

\*\* controlled-not gate

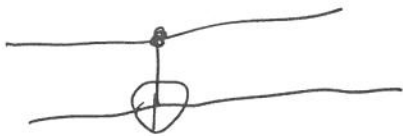



$$\begin{aligned} \text{CNOT} |00\rangle &= |00\rangle \\ \text{CNOT} |01\rangle &= |01\rangle \\ \rightarrow \text{CNOT} |10\rangle &= |11\rangle \\ \rightarrow \text{CNOT} |11\rangle &= |10\rangle \end{aligned}$$

\*\* swap gate

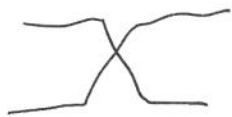


$$\text{swap} |ab\rangle = |ba\rangle$$


\*\* controlled phased gate. CZ gate

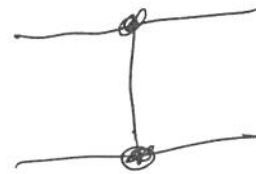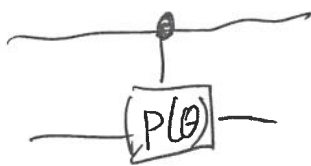

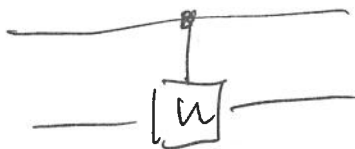\*\* if  $U$  is unitary,  $CU$  is also unitary.



\* A few more common circuits.

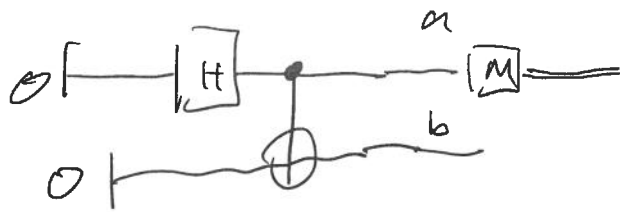

$$|00\rangle \xrightarrow{H} |+\rangle|0\rangle = \frac{1}{\sqrt{2}}(|0\rangle + |1\rangle) \otimes |0\rangle$$

$$= \frac{1}{\sqrt{2}}(|00\rangle + |10\rangle)$$

$$\xrightarrow{\text{CNOT}_{1 \rightarrow 2}} \frac{1}{\sqrt{2}}(|00\rangle + |11\rangle)$$

bell state  $\beta_{00}$ .

observation: 1. if we measure a or b, we ~~are~~ will know the value of the other.


2.  $\{\beta_{00}, \beta_{01}, \beta_{11}, \beta_{10}\}$  ~~is~~ also forms a basis for 2-qubit state.

i.e.

$$|\varphi\rangle = a\beta_{00} + b\beta_{01} + c\beta_{10} + d\beta_{11}$$

$$|a|^2 + |b|^2 + |c|^2 + |d|^2 = 1$$

\* Toffoli gate. CCX gate.

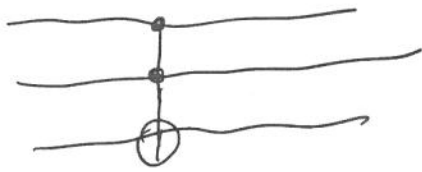


$$CCX|11a\rangle = CCX|11\bar{a}\rangle$$

otherwise

$$CCX|\psi_1, \psi_2, \psi_3\rangle = |\psi_1, \psi_2, \psi_3\rangle$$

or  $CCX|x, y, z\rangle = |x, y, (x \cdot y) \oplus z\rangle$


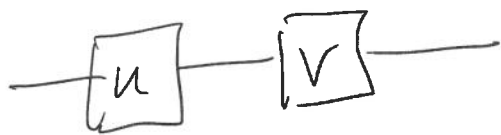
\* We can compose gates horizontally and vertically.




$$V \circ U$$



$$U \otimes V$$

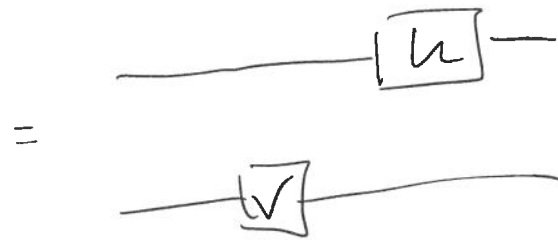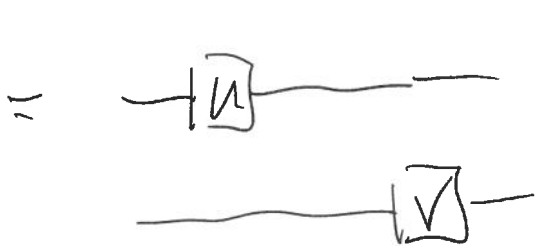


\* initialization

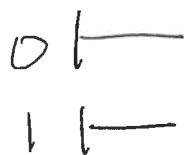

prepare a qubit in  $|0\rangle$  or  $|1\rangle$  state.

\* Termination

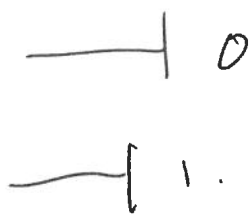

"assert" a qubit is in  $|0\rangle$  or  $|1\rangle$  state and then discard.

\* Measurement




Qubit  $\rightarrow$  Bit.

$M(a|0\rangle + b|1\rangle)$   
 returns  $|0\rangle$  with prob  $|a|^2$ .  
 $|1\rangle$  with prob  $|b|^2$ .


\* Classical circuits

Toffoli and Init/Term are enough for any classical reversible circuits!


1. Conjunction

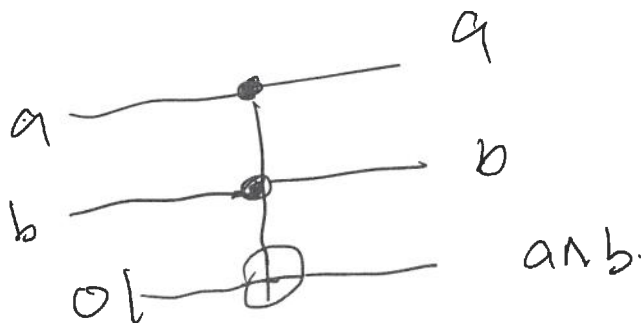

## 2. CNOT from Toffoli

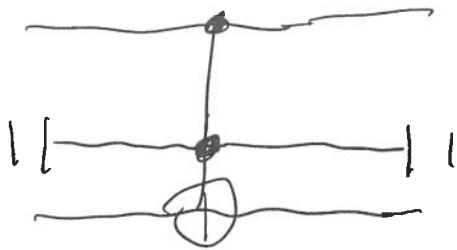

## 3. Not gate

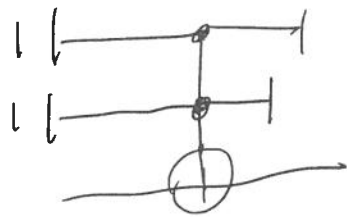


## 4. Disjunction

$$a \vee b = \neg \neg a \vee \neg \neg b \\ = \neg (\neg a \wedge \neg b)$$

---

## 5. Classical copying.

$$a \in \{|0\rangle, |1\rangle\}$$

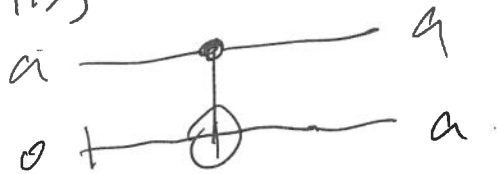


only when

$a$  is classical.  
i.e.  $a = |0\rangle$  or

$a = |1\rangle$ .

# \* Multi Controlled unitary

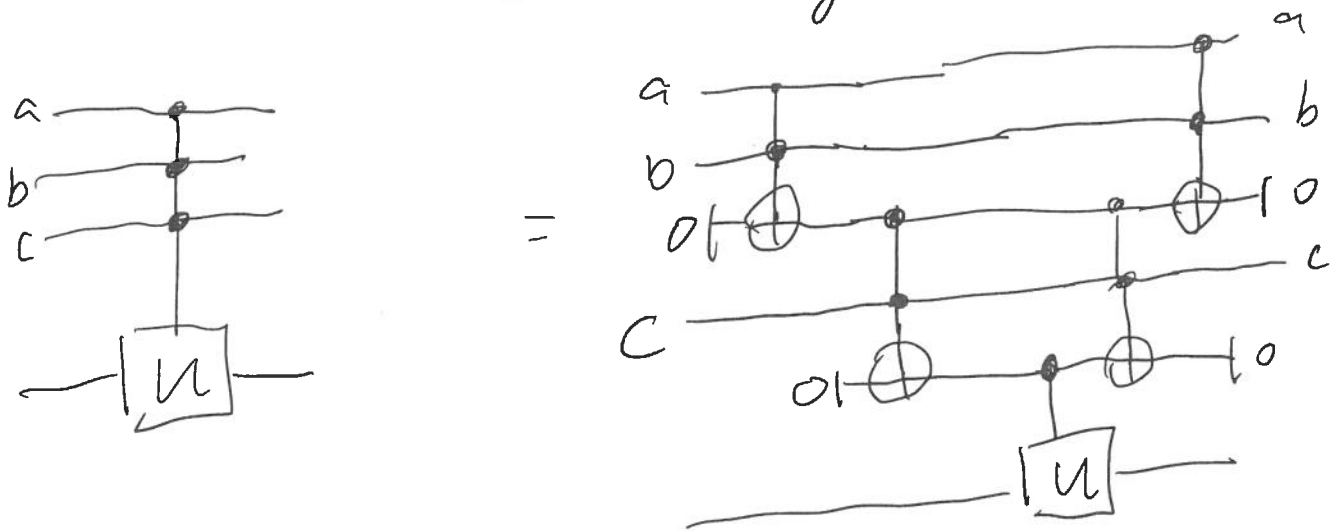

This generalizes to  $n$ -fold controls.

## \* Some useful facts and terminology

{ I, X, Y, Z, S, H, CNOT }

Clifford gate sets

Thm: Quantum circuit consisted of only Clifford gate sets and standard measurement can be efficiently implemented by Classical computer.

To achieve quantum advantage, one often works with Clifford + T gate set.

Def. A gate set is universal for quantum if Any  $n$ -Qubit unitary operation can be implemented within the gate set.

Thm. CNOT with 1-Qubit unitary is universal.

Approximating unitary.

Def. Suppose  $V$  is a unitary constructed from a finite gate set.

~~We say~~ Suppose  $U$  is a unitary.

we say  $V$  approximate  $U$  up to  $\epsilon > 0$  if  $\|U - V\| \leq \epsilon$ .